

DSD Lab 8

Register file:

```
module RegisterFile (  
    input logic [31:0] data_in, // 32-bit data input  
    input logic clk, reset, enable, // 1-bit clock, reset, enable inputs  
    output logic [31:0] data_out // 32-bit data output  
);  
    // Register to store data  
    logic [31:0] reg_data;  
  
    // Data update and reset logic  
    always_ff @(posedge clk) begin  
        if (reset) reg_data <= 32'b0; // Reset on positive edge of reset  
        else if (enable) reg_data <= data_in; // Update on enable high  
    end  
  
    // Output assignment  
    assign data_out = reg_data;  
  
endmodule
```

Test Bench:

```
module test12;  
    // Inputs  
    reg [31:0] in;  
    reg clk;  
    reg reset;  
    reg en;  
    // Outputs  
    wire [31:0] out;
```

```
// Instantiate the Unit Under Test (UUT)
```

```
register_file uut (  
    .in(in),  
    .out(out),  
    .clk(clk),  
    .reset(reset),  
    .en(en)  
);
```

```
always #5 clk = ~clk;
```

```
initial begin
```

```
// Initialize Inputs
```

```
in = 0;
```

```
clk = 0;
```

```
reset = 1;
```

```
en = 0;
```

```
#10 en = 1; reset = 0; in = 10;
```

```
#10 in = 20;
```

```
#10 in = 30;
```

```
#10 en = 0; in = 40;
```

```
#10 in = 50;
```

```
#10 in = 50;
```

```
#100 $finish;
```

```
end
```

```
endmodule
```

Example: Two bit ALU

```
module alu_2bit (
```

```
    input [1:0] A, // First 2-bit input
```

```
    input [1:0] B, // Second 2-bit input
```

```
    input [1:0] ALU_Sel, // ALU select signal
```

```
    output reg [2:0] Result // Output result (3 bits to account for carry/borrow)
```

```
);
```

```
always @(*) begin
```

```
    case(ALU_Sel)
```

```
        2'b00: Result = A & B; 2'b01: Result = A | B; 2'b10: Result = A + B; 2'b11: Result = A - B; default: Result = 3'b000;
```

```
    endcase
```

```
// AND
```

```
// OR
```

```
// ADD
```

```
// SUB
```

```
end
```

```
endmodule
```

```
module ALU_tb;

    // Testbench signals
    logic [3:0] a, b;      // 4-bit inputs
    logic [2:0] opcode;    // 3-bit operation code
    logic [3:0] result;    // 4-bit output
    logic zero;           // Zero flag

    // Instantiate the ALU module
    ALU dut (
        .a(a),
        .b(b),
        .opcode(opcode),
        .result(result),
        .zero(zero)
    );

    // Clock generation (optional, if needed for future synchronous designs)
    logic clk = 0;
    always #5 clk = ~clk;

    // Stimulus
    initial begin
        // Initialize inputs
        a = 4'b0011; b = 4'b0001; opcode = 3'b000; #10; // Add: 3 + 1 = 4
        $display("Time=%0t Add: a=%b, b=%b, result=%b, zero=%b", $time, a, b, result, zero);

        a = 4'b0010; b = 4'b0001; opcode = 3'b001; #10; // Subtract: 2 - 1 = 1
        $display("Time=%0t Subtract: a=%b, b=%b, result=%b, zero=%b", $time, a, b, result,
zero);
    end
endmodule
```

```

a = 4'b0011; b = 4'b0001; opcode = 3'b010; #10; // AND: 3 & 1 = 1
$display("Time=%0t AND: a=%b, b=%b, result=%b, zero=%b", $time, a, b, result, zero);

a = 4'b0000; b = 4'b0000; opcode = 3'b011; #10; // OR: 0 | 0 = 0
$display("Time=%0t OR: a=%b, b=%b, result=%b, zero=%b", $time, a, b, result, zero);

a = 4'b0011; b = 4'b0011; opcode = 3'b100; #10; // XOR: 3 ^ 3 = 0
$display("Time=%0t XOR: a=%b, b=%b, result=%b, zero=%b", $time, a, b, result, zero);

$finish; // End simulation
end
endmodule

```

```

// ALU Module
module ALU (
    input logic [31:0] A,
    input logic [31:0] B,
    input logic [2:0] opcode,
    output logic [31:0] result
);
    always_comb begin
        case (opcode)
            3'b000: result = 32'd0; // 0
            3'b001: result = A + B; // A + B
            3'b010: result = A - B; // A - B
            3'b011: result = A & B; // A & B
            3'b100: result = A / B; // A / B
            3'b101: result = ~A; // ~A

```

```

        3'b110: result = A;      // NoP (Assume output is same as A)
        default: result = 32'd0;
    endcase
end
endmodule

```

```

module tb_ALU;
    logic [31:0] A, B;
    logic [2:0] opcode;
    logic [31:0] result;

    ALU uut (
        .A(A),
        .B(B),
        .opcode(opcode),
        .result(result)
    );

    initial begin
        A = 32'd10; B = 32'd5;

        for (int i = 0; i < 7; i++) begin
            opcode = i[2:0];
            #10;
            $display("Opcode = %0d, Result = %0d", opcode, result);
        end

        $finish;
    end
endmodule

```

```

module RegisterFile (

```

```

input logic    clk,
input logic    reset,
input logic    RegWrite,
input logic [4:0] read_reg1,
input logic [4:0] read_reg2,
input logic [4:0] write_reg,
input logic [31:0] write_data,
output logic [31:0] read_data1,
output logic [31:0] read_data2
);
logic [31:0] registers [31:0];

// Synchronous Write on Positive Edge
always_ff @(posedge clk or posedge reset) begin
    if (reset)
        for (int i = 0; i < 32; i++)
            registers[i] <= 32'd0;
    else if (RegWrite)
        registers[write_reg] <= write_data;
end

// Asynchronous Read on Negative Edge
always_ff @(negedge clk) begin
    read_data1 <= registers[read_reg1];
    read_data2 <= registers[read_reg2];
end
endmodule

`timescale 1ns/1ps
module tb_RegisterFile;

// Testbench signals
reg    clk;

```

```

reg    reset;
reg    RegWrite;
reg [4:0] read_reg1;
reg [4:0] read_reg2;
reg [4:0] write_reg;
reg [31:0] write_data;
wire [31:0] read_data1;
wire [31:0] read_data2;

// Instantiate the RegisterFile module
RegisterFile uut (
    .clk(clk),
    .reset(reset),
    .RegWrite(RegWrite),
    .read_reg1(read_reg1),
    .read_reg2(read_reg2),
    .write_reg(write_reg),
    .write_data(write_data),
    .read_data1(read_data1),
    .read_data2(read_data2)
);

// Clock generation: 10ns period
always #5 clk = ~clk;

// Stimulus
initial begin
    // Initialize signals
    clk = 0;
    reset = 1;
    RegWrite = 0;
    read_reg1 = 0;

```

```

read_reg2 = 0;
write_reg = 0;
write_data = 0;

// Monitor the signals
$monitor("Time=%0t | Reset=%b | RegWrite=%b | WriteReg=%d | WriteData=%h |
ReadReg1=%d | ReadData1=%h | ReadReg2=%d | ReadData2=%h",
        $time, reset, RegWrite, write_reg, write_data, read_reg1, read_data1, read_reg2,
read_data2);

// Test reset
#10 reset = 0; // Release reset

// Test 1: Write to register 5 and read from it
#10 write_reg = 5; write_data = 32'hDEADBEEF; RegWrite = 1;
#10 RegWrite = 0;
#10 read_reg1 = 5; read_reg2 = 0; // Should read DEADBEEF from reg 5, 0 from reg 0

// Test 2: Write to register 10 and read from both 5 and 10
#10 write_reg = 10; write_data = 32'h12345678; RegWrite = 1;
#10 RegWrite = 0;
#10 read_reg1 = 5; read_reg2 = 10; // Should read DEADBEEF from reg 5, 12345678
from reg 10

// Test 3: Write to register 0 (should stay 0) and read
#10 write_reg = 0; write_data = 32'hFFFFFFFF; RegWrite = 1;
#10 RegWrite = 0;
#10 read_reg1 = 0; read_reg2 = 10; // Should read 0 from reg 0, 12345678 from reg 10

// Test 4: Reset and read
#10 reset = 1;
#10 reset = 0;

```



```

#10 read_reg1 = 5; read_reg2 = 10; // Should read 0 from both after reset

#20 $finish; // End simulation

end

endmodule

```

DSD Lab 7(PIPELINING)

```

module pipelined_multiplier_4x4 (

input clk,
input rst,
input [3:0] A, B,
output reg [7:0] P
);

reg [3:0] A_reg, B_reg;
reg [7:0] partial_sum1, partial_sum2;

// Stage 0: Latch inputs
always @(posedge clk or posedge rst) begin
    if (rst) begin
        A_reg <= 0;
        B_reg <= 0;
    end else begin
        A_reg <= A;
        B_reg <= B;
    end
end

// Generate partial products

```

```

wire [7:0] pp[3:0];

assign pp[0] = A_reg[0] ? {4'b0, B_reg} : 8'b0;
assign pp[1] = A_reg[1] ? {3'b0, B_reg, 1'b0} : 8'b0;
assign pp[2] = A_reg[2] ? {2'b0, B_reg, 2'b0} : 8'b0;
assign pp[3] = A_reg[3] ? {1'b0, B_reg, 3'b0} : 8'b0;

// Stage 1: Add first two and last two partial products
always @(posedge clk or posedge rst) begin
    if (rst)
        partial_sum1 <= 0;
    else
        partial_sum1 <= pp[0] + pp[1];
end

always @(posedge clk or posedge rst) begin
    if (rst)
        partial_sum2 <= 0;
    else
        partial_sum2 <= pp[2] + pp[3];
end

// Stage 2: Final sum
always @(posedge clk or posedge rst) begin
    if (rst)
        P <= 0;
    else
        P <= partial_sum1 + partial_sum2;
end

endmodule

```

```
`timescale 1ns/1ps

module tb_pipelined_multiplier_4x4;

    reg clk, rst;
    reg [3:0] A, B;
    wire [7:0] P;

    pipelined_multiplier_4x4 uut (
        .clk(clk),
        .rst(rst),
        .A(A),
        .B(B),
        .P(P)
    );

    always #5 clk = ~clk;

    initial begin
        clk = 0;
        rst = 1;
        A = 0;
        B = 0;

        $monitor("Time = %0t | A = %d, B = %d => P = %d", $time, A, B, P);

        #10 rst = 0;
        #10 A = 4'd3; B = 4'd5;
        #10 A = 4'd15; B = 4'd15;
        #10 A = 4'd7; B = 4'd2;
        #10 A = 4'd0; B = 4'd12;
```

```
#50 $stop;  
end
```

```
endmodule
```

```
module pipelined_4bit_adder_2stage (  
    input logic    clk,  
    input logic    rst,  
    input logic [3:0] A,  
    input logic [3:0] B,  
    output logic [3:0] SUM,  
    output logic    COUT  
);  
  
    // First stage outputs  
    logic s0, s1, c1;  
  
    // Pipeline registers (between stage 1 and 2)  
    logic [1:0] sum_stage1;  
    logic    carry_stage1;  
    logic [1:0] a_high, b_high;  
  
    // Stage 1: Add bit 0 and bit 1  
    always_ff @(posedge clk or posedge rst) begin  
        if (rst) begin  
            sum_stage1  <= 2'b00;  
            carry_stage1 <= 1'b0;  
            a_high      <= 2'b00;  
        end  
    end
```

```

    b_high    <= 2'b00;
end else begin
    // Full Adder for bit 0
    s0 = A[0] ^ B[0];
    logic c0 = A[0] & B[0];

    // Full Adder for bit 1
    s1 = A[1] ^ B[1] ^ c0;
    c1 = (A[1] & B[1]) | (A[1] & c0) | (B[1] & c0);

    // Store sum and carry in pipeline registers
    sum_stage1  <= {s1, s0};
    carry_stage1 <= c1;
    a_high     <= A[3:2];
    b_high     <= B[3:2];
end
end

// Stage 2: Add bit 2 and bit 3
logic s2, s3;
logic c2, c3;

always_ff @(posedge clk or posedge rst) begin
    if (rst) begin
        SUM <= 4'b0000;
        COUT <= 1'b0;
    end else begin
        // Full Adder for bit 2
        s2 = a_high[0] ^ b_high[0] ^ carry_stage1;
        c2 = (a_high[0] & b_high[0]) | (a_high[0] & carry_stage1) | (b_high[0] &
carry_stage1);

```

```

        // Full Adder for bit 3
        s3 = a_high[1] ^ b_high[1] ^ c2;
        c3 = (a_high[1] & b_high[1]) | (a_high[1] & c2) | (b_high[1] & c2);

        // Output result
        SUM <= {s3, s2, sum_stage1};
        COUT <= c3;
    end
end

endmodule

```

```

module pipelined_4bit_ripple_carry_adder (
    input logic    clk,
    input logic    rst,
    input logic [3:0] A,
    input logic [3:0] B,
    output logic [3:0] SUM,
    output logic    COUT
);

```

```

    // Stage 1 Registers
    logic s0, c0;
    logic a0, b0;

```

```

    // Stage 2 Registers
    logic s1, c1;
    logic a1, b1;

```

```

// Stage 3 Registers
logic s2, c2;
logic a2, b2;

// Stage 4 Registers
logic s3;
logic a3, b3;
logic cout_reg;

// Register inputs
always_ff @(posedge clk or posedge rst) begin
    if (rst) begin
        {a0, b0, a1, b1, a2, b2, a3, b3} <= 8'b0;
    end else begin
        a0 <= A[0]; b0 <= B[0];
        a1 <= A[1]; b1 <= B[1];
        a2 <= A[2]; b2 <= B[2];
        a3 <= A[3]; b3 <= B[3];
    end
end

// Stage 1: Add LSBs
always_ff @(posedge clk or posedge rst) begin
    if (rst) begin
        s0 <= 0; c0 <= 0;
    end else begin
        s0 <= a0 ^ b0;
        c0 <= a0 & b0;
    end
end

// Stage 2

```

```

always_ff @(posedge clk or posedge rst) begin
    if (rst) begin
        s1 <= 0; c1 <= 0;
    end else begin
        s1 <= a1 ^ b1 ^ c0;
        c1 <= (a1 & b1) | (a1 & c0) | (b1 & c0);
    end
end

```

// Stage 3

```

always_ff @(posedge clk or posedge rst) begin
    if (rst) begin
        s2 <= 0; c2 <= 0;
    end else begin
        s2 <= a2 ^ b2 ^ c1;
        c2 <= (a2 & b2) | (a2 & c1) | (b2 & c1);
    end
end

```

// Stage 4

```

always_ff @(posedge clk or posedge rst) begin
    if (rst) begin
        s3 <= 0; cout_reg <= 0;
    end else begin
        s3 <= a3 ^ b3 ^ c2;
        cout_reg <= (a3 & b3) | (a3 & c2) | (b3 & c2);
    end
end

```

// Output

```

assign SUM = {s3, s2, s1, s0};
assign COUT = cout_reg;

```



```
endmodule
```

FSM

```
module consec(z,clk,rst,in);
input clk,rst,in;
output reg z;
reg [3:0]cs,ns;

//(* fsm_encoding = "gray" *) reg [3:0] cs,ns;
always@(posedge clk) begin
if (rst) begin
cs <= 4'b0000;
end else begin
cs <= ns;
end
end

always@(*) begin
case(cs)

4'b0000:
begin
z=0;
if(in==0)
ns=4'b0101;
```

```
else  
ns=4'b0001;  
end
```

```
4'b0001:  
begin  
z=0;  
if(in==0)  
ns=4'b0101;  
else  
ns=4'b0010;  
end
```

```
4'b0010:  
begin  
z=0;  
if(in==0)  
ns=4'b0101;  
else  
ns=4'b0011;  
end
```

```
4'b0011:  
begin  
z=0;  
if(in==0)  
ns=4'b0101;  
else  
ns=4'b0100;  
end
```

```
4'b0100:
```

```
begin
z=1;
if(in==0)
ns=4'b0101;
else begin
ns=4'b0100;
end
end
```

```
4'b0101:
begin
z=0;
if(in==0)
ns=4'b0110;
else
ns=4'b0001;
end
```

```
4'b0110:
begin
z=0;
if(in==0)
ns=4'b0111;
else
ns=4'b0001;
end
```

```
4'b0111:
begin
z=0;
if(in==0)
ns=4'b1000;
```

```
else
ns=4'b0001;
end
```

```
4'b1000:
begin
z=1;
if(in==0)begin
ns=4'b1000;
end
else
ns=4'b0001;
end
```

```
default:
begin
z=0;
ns=0;
end
```

```
endcase
end
```

```
endmodule
```

```
module task2(z,clk,rst,w);
input clk,rst,w;
output reg z;
```

```
reg [3:0]store,store2;
```

```
always@(posedge clk) begin
```

```
if (rst) begin
```

```
store <= 0;
```

```
store2<=0;
```

```
z <= 0;
```

```
end
```

```
else
```

```
store<= {store,w};
```

```
store2<= {store2,w};
```

```
if (store == 4'b0000 || store2 == 4'b1111) begin
```

```
z <= 1;
```

```
end
```

```
else
```

```
z <= 0;
```

```
end
```

```
endmodule
```

Zero_99

```
module zero_99(
```

```
    input clock,
```

```
    input reset,
```

```
    output a, b, c, d, e, f, g,
```

```
    output dp,
```

```

output [7:0] an
);
reg [3:0] first; // Units digit (0-9)
reg [3:0] second; // Tens digit (0-9)
reg [23:0] delay; // For 0.1-second delay
wire test;

// Delay counter for 0.1-second updates
always @(posedge clock or posedge reset) begin
    if (reset) delay <= 0;
    else delay <= delay + 1;
end
assign test = &delay; // High when delay overflows

// Counter logic: Increment digits every 0.1 second
always @(posedge test or posedge reset) begin
    if (reset) begin
        first <= 0;
        second <= 0;
    end else if (first == 4'd9) begin
        first <= 0;
        if (second == 4'd9) second <= 0;
        else second <= second + 1;
    end else first <= first + 1;
end

// Multiplexing for 4-digit display
localparam N = 18;
reg [N-1:0] count;
always @(posedge clock or posedge reset) begin
    if (reset) count <= 0;
    else count <= count + 1;
end

```

end

reg [6:0] sseg;

reg [7:0] an_temp;

always @(*) begin

case(count[N-1:N-2])

2'b00: begin

sseg = first;

an_temp = 8'b11111110;

end

2'b01: begin

sseg = second;

an_temp = 8'b11111101;

end

2'b10: begin

sseg = 6'ha;

an_temp = 8'b11111011;

end

2'b11: begin

sseg = 6'ha;

an_temp = 8'b11110111;

end

endcase

end

assign an = an_temp;

// 7-segment display encoding

reg [6:0] sseg_temp;

always @(*) begin

case(sseg)

4'd0: sseg_temp = 7'b1000000;

4'd1: sseg_temp = 7'b1111001;

```

4'd2: sseg_temp = 7'b0100100;
4'd3: sseg_temp = 7'b0110000;
4'd4: sseg_temp = 7'b0011001;
4'd5: sseg_temp = 7'b0010010;
4'd6: sseg_temp = 7'b0000010;
4'd7: sseg_temp = 7'b1111000;
4'd8: sseg_temp = 7'b0000000;
4'd9: sseg_temp = 7'b0010000;
default: sseg_temp = 7'b0111111;
endcase
end
assign {g, f, e, d, c, b, a} = sseg_temp;
assign dp = 1'b1;
endmodule

```

Z_99_up_down

```

always_ff @(posedge clk or posedge rst)begin
    if(rst)
        begin
            f<=0;
            s<=0;
        end

    else if (up_enable)
        begin
            if(f==4'b9)
                begin
                    f<=0;
                    if(s==4'b9)
                        s<=0;
                    else
                        s<=s+1;
                end
            else

```



```

    f<=f+1;
end

else if (down_enable)
begin

    if(f==4'b0)
begin
        f<=9;
        if(s==4'b0)
            s<=9;
        else
            s<=s-1;
        end
    else
        f<=f-1;
    end

    else begin
        s <= s;
        f <= f;
    end
end
end

```

Digital_CLocl_CODE

```

module segments(
    input [5:0] number,      // 6-bit input (0 to 30)
    output reg [13:0] segments // 14-bit output for two 7-segment displays
);
    always @*
        case(number)
            6'd00: segments = 14'b01111111_01111111; // 0
            6'd01: segments = 14'b01111111_00001110; // 1
            6'd02: segments = 14'b01111111_10110111; // 2
            6'd03: segments = 14'b01111111_10011111; // 3
            6'd04: segments = 14'b01111111_11001110; // 4
            6'd05: segments = 14'b01111111_11011011; // 5
            6'd06: segments = 14'b01111111_11111011; // 6
            6'd07: segments = 14'b01111111_00001111; // 7
        endcase
endmodule

```

```

6'd08: segments = 14'b0111111_1111111; // 8
6'd09: segments = 14'b0111111_1101111; // 9
6'd10: segments = 14'b0000110_0111111; // 10
6'd11: segments = 14'b0000110_0000110; // 11
6'd12: segments = 14'b0000110_1011011; // 12
6'd13: segments = 14'b0000110_1001111; // 13
6'd14: segments = 14'b0000110_1100110; // 14
6'd15: segments = 14'b0000110_1101101; // 15
6'd16: segments = 14'b0000110_1111101; // 16
6'd17: segments = 14'b0000110_0000111; // 17
6'd18: segments = 14'b0000110_1111111; // 18
6'd19: segments = 14'b0000110_1101111; // 19
6'd20: segments = 14'b1011011_0111111; // 20
6'd21: segments = 14'b1011011_0000110; // 21
6'd22: segments = 14'b1011011_1011011; // 22
6'd23: segments = 14'b1011011_1001111; // 23
6'd24: segments = 14'b1011011_1100110; // 24
6'd25: segments = 14'b1011011_1101101; // 25
6'd26: segments = 14'b1011011_1111101; // 26
6'd27: segments = 14'b1011011_0000111; // 27
6'd28: segments = 14'b1011011_1111111; // 28
6'd29: segments = 14'b1011011_1101111; // 29
6'd30: segments = 14'b1001111_0111111; // 30
endcase
endmodule

```

```

module clock(
    input clk,          // 100 MHz FPGA clock
    input reset,        // Resets the clock
    output reg [6:0] segments,
    output reg [7:0] anodes // Controls active digit
);
    reg [32:0] count; // Clock divider counter
    reg clr_count;

    reg [4:0] sec; // Seconds (0-30, 5 bits)
    reg clr_sec;

    reg [2:0] min; // Minutes (0-7, 3 bits)
    reg clr_min;

    reg [2:0] hrs; // Hours (0-7, 3 bits)
    reg clr_hrs;

    wire [6:0] sec_mss, sec_1ss; // Tens and ones of seconds
    wire [6:0] mins_mss, mins_1ss; // Tens and ones of minutes

```

```

wire [6:0] hrs_mss, hrs_iss; // Tens and ones of hours

reg [31:0] seg_count; // Multiplexing counter

// Clock divider
always @(posedge clk)
    if (reset || clr_count) count <= #1 0;
    else count <= #1 count + 1;
always @* clr_count = (count == 33'd99_999_999); // ~1 second

// Seconds counter
always @(posedge clk)
    if (reset || clr_sec) sec <= #1 0;
    else if (clr_count) sec <= #1 sec + 1;
always @* clr_sec = clr_count & (sec == 6'd30); // Reset at 30 seconds

// Minutes counter
always @(posedge clk)
    if (reset || clr_min) min <= #1 0;
    else if (clr_sec) min <= #1 min + 1;
always @* clr_min = clr_sec & (min == 5'd2); // Reset at 2 minutes

// Hours counter
always @(posedge clk)
    if (reset || clr_hrs) hrs <= #1 0;
    else if (clr_min) hrs <= #1 hrs + 1;
always @* clr_hrs = clr_sec & (min == 5'd2) & (hrs == 5'd2); // Reset at 2 hours

// Segment generation
segments sec_seg (.number({1'b0, sec}), .segments({sec_mss, sec_iss}));
segments mins_seg (.number({3'b0, min}), .segments({mins_mss, mins_iss}));
segments hrs_seg (.number({3'b0, hrs}), .segments({hrs_mss, hrs_iss}));

// Multiplexing counter
always @(posedge clk)
    if (reset) seg_count <= #1 0;
    else seg_count <= #1 seg_count + 1;

// Segment selection
always @*
    case (seg_count[19:17])
        3'd0: segments = ~sec_iss; // Ones of seconds
        3'd1: segments = ~sec_mss; // Tens of seconds
        3'd2: segments = ~mins_iss; // Ones of minutes
        3'd3: segments = ~mins_mss; // Tens of minutes
        3'd4: segments = ~hrs_iss; // Ones of hours
        3'd5: segments = ~hrs_mss; // Tens of hours
    endcase

```

```

        default: segments = 0;
    endcase

// Anode control
always @*
    case (seg_count[19:17])
        3'd0: anodes = 8'b11111110; // Digit 0
        3'd1: anodes = 8'b11111101; // Digit 1
        3'd2: anodes = 8'b11111011; // Digit 2
        3'd3: anodes = 8'b11110111; // Digit 3
        3'd4: anodes = 8'b11101111; // Digit 4
        3'd5: anodes = 8'b11011111; // Digit 5
        default: anodes = 8'b11111111;
    endcase
endmodule

```

OPT_CLoCk_CODE

```
`timescale 1ns / 1ps
```

```

module clock_2(
    input clk,          // Main clock signal
    input reset,        // Reset signal
    output reg [6:0] ssd, // Seven-segment display output
    output reg [7:0] anode // Anode output for multiplexing
);

    reg [25:0] count; // Counter for generating 1Hz clock
    reg clk_1hz;      // 1Hz clock signal
    reg [3:0] sec_1ss; // Least significant second digit
    reg [3:0] sec_mss; // Most significant second digit
    reg [3:0] min_1ss; // Least significant minute digit
    reg [3:0] min_mss; // Most significant minute digit
    reg [3:0] hr_1ss;  // Least significant hour digit
    reg [3:0] hr_mss;  // Most significant hour digit
    reg [19:0] seg_count; // Counter for segment multiplexing
    reg [3:0] number;    // Digit to be displayed

    // Generate 1Hz clock from 100MHz clock

```

```

always @(posedge clk or posedge reset) begin
    if (reset) begin
        count <= 0;
        clk_1hz <= 0;
    end else if (count == 50_000_000) begin
        clk_1hz <= ~clk_1hz;
        count <= 0;
    end else begin
        count <= count + 1;
    end
end
end

```

```

// Clock logic for seconds, minutes, and hours
always @(posedge clk_1hz or posedge reset) begin
    if (reset) begin
        sec_lss <= 0;
        sec_mss <= 0;
        min_lss <= 0;
        min_mss <= 0;
        hr_lss <= 0;
        hr_mss <= 0;
    end else begin
        if (sec_lss == 9) begin
            sec_lss <= 0;
            if (sec_mss == 5) begin
                sec_mss <= 0;
                if (min_lss == 9) begin
                    min_lss <= 0;
                    if (min_mss == 5) begin
                        min_mss <= 0;
                        if (hr_lss == 3 && hr_mss == 2) begin
                            hr_lss <= 0;
                            hr_mss <= 0;
                        end else if (hr_lss == 9) begin
                            hr_lss <= 0;
                            hr_mss <= hr_mss + 1;
                        end else begin
                            hr_lss <= hr_lss + 1;
                        end
                    end else begin
                        min_mss <= min_mss + 1;
                    end
                end else begin
                    min_lss <= min_lss + 1;
                end
            end else begin
                sec_mss <= sec_mss + 1;
            end
        end
    end
end

```

```

        end
    end else begin
        sec_lss <= sec_lss + 1;
    end
end
end

// Multiplexing logic for seven-segment display
always @(posedge clk) begin
    seg_count <= seg_count + 1;
end

always @(*) begin
    case (seg_count[19:17])
        3'd0: begin
            number = sec_lss; // Display least significant second digit
            anode = 8'b11111110;
        end
        3'd1: begin
            number = sec_mss; // Display most significant second digit
            anode = 8'b11111101;
        end
        3'd2: begin
            number = min_lss; // Display least significant minute digit
            anode = 8'b11111011;
        end
        3'd3: begin
            number = min_mss; // Display most significant minute digit
            anode = 8'b11110111;
        end
        3'd4: begin
            number = hr_lss; // Display least significant hour digit
            anode = 8'b11101111;
        end
        3'd5: begin
            number = hr_mss; // Display most significant hour digit
            anode = 8'b11011111;
        end
        default: begin
            number = 4'b1111; // Turn off all segments
            anode = 8'b11111111;
        end
    endcase
end

// Seven-segment display encoding
always @(*) begin

```

```
case (number)
  4'd0: ssd = 7'b1000000; // 0
  4'd1: ssd = 7'b1111001; // 1
  4'd2: ssd = 7'b0100100; // 2
  4'd3: ssd = 7'b0110000; // 3
  4'd4: ssd = 7'b0011001; // 4
  4'd5: ssd = 7'b0010010; // 5
  4'd6: ssd = 7'b0000010; // 6
  4'd7: ssd = 7'b1111000; // 7
  4'd8: ssd = 7'b0000000; // 8
  4'd9: ssd = 7'b0010000; // 9
  default: ssd = 7'b1111111; // Turn off all segments
endcase
end

endmodule
```

```
wsl --install
```

```
curl -fsSL https://ollama.com/install.sh | sh
```

```
ollama pull llama3.2:1b
```

```
ollama run llama3.2:1b "What is the capital of France?"
```